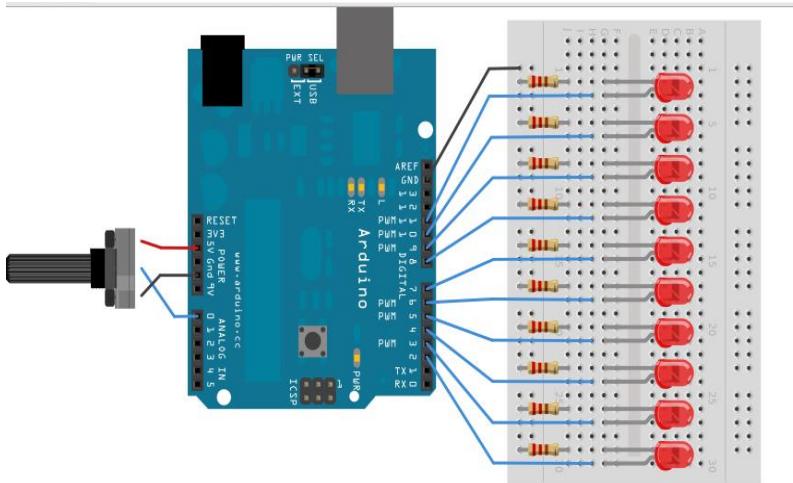


Diseña los siguientes circuitos en 123d circuits y programa el arduino para su funcionamiento:


Circuito 1:



Hardware Required

- Arduino or Genuino Board
- LED bar graph display or 10 LEDs
- Potentiometer
- 10 220 ohm resistors
- hook-up wires
- breadboard

Schematic:

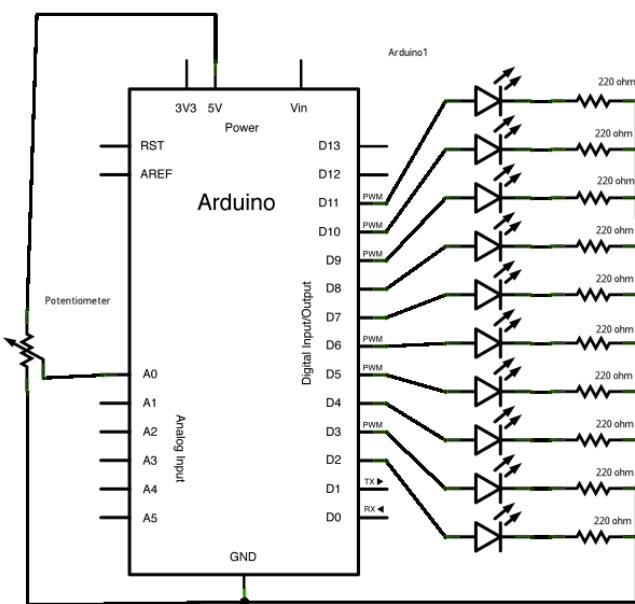


Code

```
// these constants won't change:  
const int analogPin = A0;    // the pin that the potentiometer is attached to  
const int ledCount = 10;     // the number of LEDs in the bar graph  
  
int ledPins[] = {  
  2, 3, 4, 5, 6, 7, 8, 9, 10, 11  
};  // an array of pin numbers to which LEDs are attached  
  
void setup() {  
  // loop over the pin array and set them all to output:  
  for (int thisLed = 0; thisLed < ledCount; thisLed++) {  
    pinMode(ledPins[thisLed], OUTPUT);  
  }  
}  
  
void loop() {  
  // read the potentiometer:  
  int sensorReading = analogRead(analogPin);  
  // map the result to a range from 0 to the number of LEDs:  
  int ledLevel = map(sensorReading, 0, 1023, 0, ledCount);
```

```
// loop over the LED array:  
for (int thisLed = 0; thisLed < ledCount; thisLed++) {  
  // if the array element's index is less than ledLevel,  
  // turn the pin for this element on:  
  if (thisLed < ledLevel) {  
    digitalWrite(ledPins[thisLed], HIGH);  
  }  
  // turn off all pins higher than the ledLevel:  
  else {  
    digitalWrite(ledPins[thisLed], LOW);  
  }  
}
```

Circuito 2:

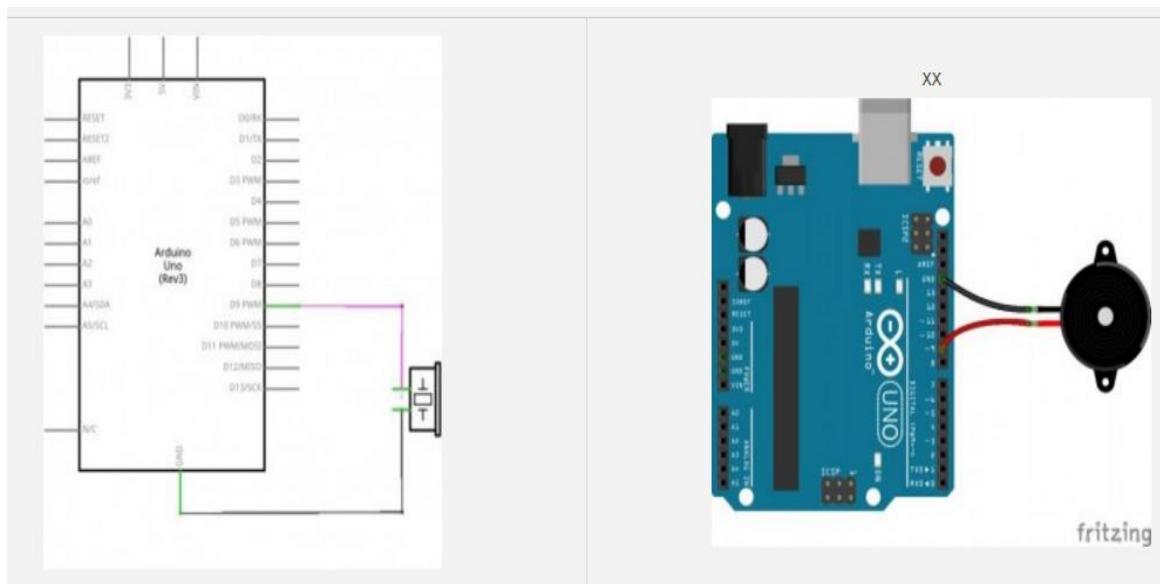

Hardware Required

- Arduino or Genuino Board
- Buzzer
- hook-up wires
- breadboard

Code

```
void beep(unsigned char pausa)
{
    analogWrite(9, 20);
    delay(pausa); // Espera
    analogWrite(9, 0); // Apaga
    delay(pausa); // Espera
}
```

```
void setup()
{
    pinMode(9, OUTPUT);
    beep(50);
    beep(50);
    beep(50);
    delay(1000);
}

void loop()
{
    beep(200);
}
```